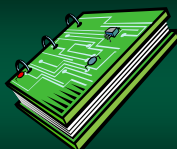


Arbitrary Circuits

Part 12

1




Creating an Arbitrary Circuit

From Truth Table to Wires

2

Creating an Arbitrary Circuit

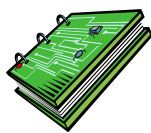- We converted between Boolean expressions and circuits
- It maintained a one-to-one correspondence between gates in the circuit and operators in the equation




Spring 2020 Sacramento State - Cook - CSc 28 3

3

Creating an Arbitrary Circuit

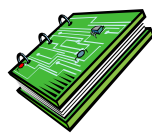
- Given an arbitrary logic table, how do we realize a circuit for it?
- Simple, we look at the inputs that make it true, and write them out in an expression using or's.



Spring 2020 Sacramento State - Cook - CSc 28 4

4

Example: 1 Bit Add Mod 2

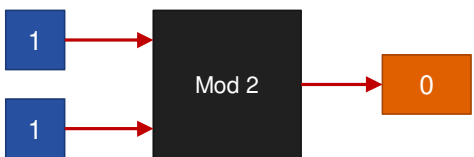

Spring 2020 Sacramento State - Cook - CSc 28 5

5

Example: 1 Bit Add Mod 2

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Spring 2020 Sacramento State - Cook - CSc 28 6

6

Example: 1 Bit Add Mod 2

We want a circuit that is true when:

$(a = \text{F} \text{ and } b = \text{T}) \text{ or } (a = \text{T} \text{ and } b = \text{F})$

$\text{out} = a' * b + a * b'$


Spring 2020

Sacramento State - Cook - CSc 28

7

7

Example 2: One Bit Adder

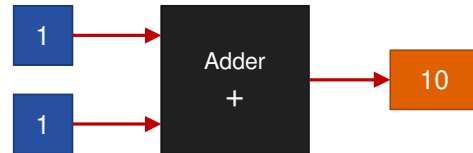

Spring 2020

Sacramento State - Cook - CSc 28

8

8

Example 2: One Bit Adder

a	b	Out ₁	Out ₀
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Spring 2020

Sacramento State - Cook - CSc 28

9

9

Example: One Bit Adder (Logic)

$\text{out1} = (a = \text{T} \text{ and } b = \text{T})$

$\text{out0} = (a = \text{F} \text{ and } b = \text{T}) \text{ or } (a = \text{T} \text{ and } b = \text{F})$

Spring 2020

Sacramento State - Cook - CSc 28

10

10

Example: One Bit Adder (algebra)

$\text{out1} = a * b$

$\text{out0} = a' * b + a * b'$

Spring 2020

Sacramento State - Cook - CSc 28

11

11




Disjunctive Normal Form

Express Logic With Ease

12

Disjunctive Normal Form

- Best approach to converting tables into circuits is use *Disjunctive Normal Form*
- In this form, the expressions consists of OR's (disjuncts) connecting AND sub-expressions

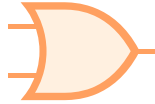

Spring 2020


Sacramento State - Cook - CSc 28

13

13

Definitions

- A *literal* is a Boolean variable v or its complement (e.g. v or v')
- A *minterm* of Boolean product $v_1 * v_2 * \dots * v_n$

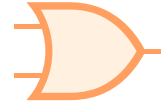


Spring 2020

Sacramento State - Cook - CSc 28

14

14

Definitions

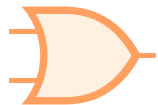

- Hence, a minterm is a "product" of n literals, with one literal for each variable
- An equation written only as the "OR" of minterms is in *disjunctive normal form* (also called *sum-of-products* form)

Spring 2020

Sacramento State - Cook - CSc 28

15

15

Algorithm

- Find the rows that indicates a 1 for output
 - ignore the ones with 0 as output
 - we are making an equation based on true
- Write a minterm for each of them
- "OR" all the minterms

Spring 2020

Sacramento State - Cook - CSc 28

16

16

Example

a	b	y (out)
0	0	1
0	1	1
1	0	0
1	1	0

Spring 2020

Sacramento State - Cook - CSc 28

17

17

Example

DNF of the table is:

$$y = (a' * b') + (a' * b)$$

For brevity, for this point on, let's write as:

$$y = a'b' + a'b$$

Spring 2020

Sacramento State - Cook - CSc 28

18

18


Example

We can simply using Boolean algebra:

$$\begin{aligned}
 y &= a'b' + a'b \\
 &= a' (b' + b) && \text{Distributive} \\
 &= a' (1) && \text{Complement} \\
 &= a' && \text{Identity}
 \end{aligned}$$

Spring 2020 Sacramento State - Cook - CSc 28 19

19

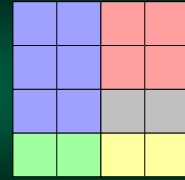

Karnaugh Maps


The Right-Brain Gets to Help

Spring 2020 Sacramento State - Cook - CSc 28 20

20

Karnaugh Maps

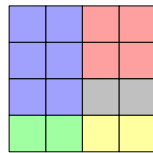- A *Karnaugh Map* (pronounced "car-no") is a visual tool to help see relations between minterms.
- A K-Map for n variables is a grid of 2^n squares




Spring 2020 Sacramento State - Cook - CSc 28 21

21

Karnaugh Maps

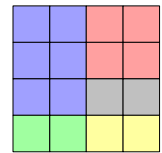- Every possible minterm of n variables is represented
- Every square is a minterm*
- It is arranged in such a way that we can simplify our table



Spring 2020 Sacramento State - Cook - CSc 28 22

22

Gray Code

- Literals are ordered using *gray code*
 - values in the table are not ordered in normal ascending order
 - each square differs in exactly *one* literal
 - why? we will cover this later
- NOTE:** squares wrap-around to the sides

Spring 2020 Sacramento State - Cook - CSc 28 23

23


Two Variable Example

a	b	out
0	0	1
0	1	1
1	0	1
1	1	0

Spring 2020 Sacramento State - Cook - CSc 28 24

24

Two Variable K-Map

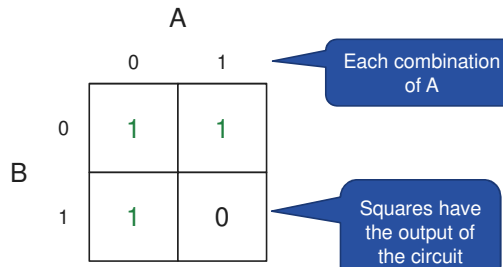

Spring 2020

Sacramento State - Cook - CSc 28

25

25

Three Variable Example

a	b	c	out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Spring 2020

Sacramento State - Cook - CSc 28

26

26

Three Variable K-Map

AB

	00	01	11	10
0	1	0	1	1
1	0	0	1	1

C

Spring 2020

Sacramento State - Cook - CSc 28

27

27

Four Variable K-Map

AB

	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	1	0
10	0	1	1	0

CD

Spring 2020

Sacramento State - Cook - CSc 28

28

28

How to Use a K-Map

1. Mark the squares of a K-map corresponding to the function
2. Select a minimal set of rectangles where
 - each rectangle has a **power-of-two area** and is as large as possible
 - cover every marked square
3. Translate each rectangle into a single midterm and sum (or) all these

Spring 2020

Sacramento State - Cook - CSc 28

29

29

Converting a Rectangle to Minterm



- If any literal contains both 1 and 0, in the rectangle, it is **eliminated**
- The goal is to draw the **biggest** rectangles possible

Spring 2020

Sacramento State - Cook - CSc 28

30

30

Example Square: 1×1

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$A' B C' D$
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

31

31

Example Square: 2×1

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$B C' D$
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

32

32

Example Square: 1×4

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$C' D$
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

33

33

Example Square: 2×2

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$A' D$
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

34

34

Example Square: 2×2: Wrapped

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$B' D$
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

35

35

Example Square: 2×2: Wrapped

		AB				
		00	01	11	10	
CD	00	1	0	0	1	$B' D'$
	01	1	1	1	1	
	11	1	1	0	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

36

36

Example Square: 4x2

		AB				
		00	01	11	10	
CD	00	1	0	0	1	D
	01	1	1	1	1	
	11	1	1	1	1	
	10	1	0	0	1	

Spring 2020

Sacramento State - Cook - CSc 28

37

37

Tips

- There is no magic way to do Step 2. Look and play around until you find the answer
- You can overlap squares – just as long as you "cover" all the 1's



Spring 2020

Sacramento State - Cook - CSc 28

38

38

Four-Variable K-Map

		AB				
		00	01	11	10	
CD	00	0	0	1	1	$A'D + BC + AC'D'$
	01	1	1	0	0	
	11	1	1	1	0	
	10	0	1	1	0	

Spring 2020

Sacramento State - Cook - CSc 28

39

39

Efficiency of K-Maps

- A K-Map does not necessarily make the **best** expression/circuit
- All expressions made this way are sums-of-products and some can be made simpler
- For example: $a(b+c)$ is the same as $ab+ac$, but uses fewer gate inputs


Spring 2020

Sacramento State - Cook - CSc 28

40

40


How K-Maps Work

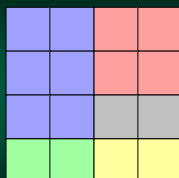

You are doing more than you think

How K-Maps Work

- The order of gray code, and the 2^n squares allow us to factor out literals
- Every time you eliminate a literal, you are performing **three** Boolean algebra laws
- This is done visually, so it is invisible!

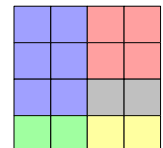

Spring 2020

Sacramento State - Cook - CSc 28

42

42

How K-Maps Work

1. First you use the *Distribution Law* on the minterms leaving $(v + v')$ - which is the terminal that *changed*
2. You then use the *Complement Law* on $(v + v')$ leaving 1
3. Finally, you remove the 1 using the *Identity Law*


Spring 2020

Sacramento State - Cook - CSc 28

43

43

Let's Look at This Again...

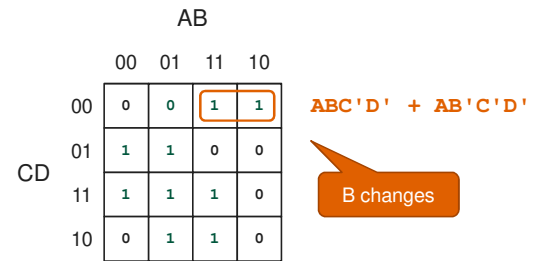

Spring 2020

Sacramento State - Cook - CSc 28

44

44

Let's Look at This Again...

$$ABC'D' + AB'C'D'$$

$$AC'D'(B + B') \quad \text{Distributive}$$

$$AC'D'(1) \quad \text{Complement}$$

$$AC'D' \quad \text{Identity}$$


Spring 2020

Sacramento State - Cook - CSc 28

45

45

How About Another Rectangle?

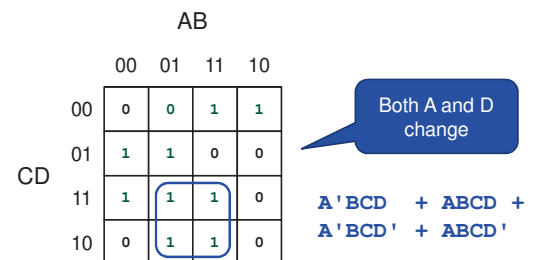

Spring 2020

Sacramento State - Cook - CSc 28

46

46

How About Another Rectangle?

$$A'BCD + ABCD + A'BCD' + ABCD'$$

$$BCD(A' + A) + BCD'(A' + A)$$

$$BCD(1) + BCD'(1)$$

$$BCD + BCD' \quad \text{A eliminated}$$

Spring 2020

Sacramento State - Cook - CSc 28

47

47

... and it keeps going...

$$BCD + BCD'$$

$$BC(D + D')$$

$$BC(1)$$

$$BC \quad \text{D eliminated}$$

Spring 2020

Sacramento State - Cook - CSc 28

48

48




Please Wait

CSC 28
will begin shortly

Please open the chat
window.

49




K-Maps and Programming

Using it to simplify code

50

K-Maps and Programming

- The Boolean expressions, that you use in your Java programs, are the same as the expressions we cover
- So, you can apply K-Maps to your Java code to simplify expressions



Spring 2020 Sacramento State - Cook - CSC 28 51

51

K-Maps Can Simplify Expressions

- The following is a complex expression that, on the surface, looks difficult to simplify
- K-Maps can help

```
if (a && !b && c || a && b && !c ||
    a && !b && !c || a && b && c)
```

Spring 2020 Sacramento State - Cook - CSC 28 52

52

K-Maps Can Simplify Expressions

- First, let's put the expression in the Computer Engineer notation
- Ah, we can see the structure now!

```
ab'c' + abc' + ab'c + abc
```

Spring 2020 Sacramento State - Cook - CSC 28 53

53

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0				
	1				

```
ab'c' + abc' + ab'c + abc
```

Spring 2020 Sacramento State - Cook - CSC 28 54

54

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0				1
	1				

$$ab'c' + abc' + ab'c + abc$$

Spring 2020

Sacramento State - Cook - CSc 28

55

55

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1				

$$ab'c' + abc' + ab'c + abc$$

Spring 2020

Sacramento State - Cook - CSc 28

56

56

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1				1

$$ab'c' + abc' + ab'c + abc$$

Spring 2020

Sacramento State - Cook - CSc 28

57

57

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1			1	1

$$ab'c' + abc' + ab'c + abc$$

Spring 2020

Sacramento State - Cook - CSc 28

58

58

K-Maps Can Simplify Expressions

		ab			
		00	01	11	10
c	0			1	1
	1			1	1

$$ab'c' + abc' + ab'c + abc = a$$

Spring 2020

Sacramento State - Cook - CSc 28

59


59



60

Don't Care

- Sometimes *we don't really care* what output the circuit generates for some combinations of inputs
- So, for those inputs, the results are simply not significant

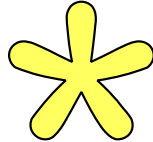

Spring 2020


Sacramento State - Cook - CSc 28

61

61

Don't Care

- In truth tables, the value "Don't Care" is represented with an asterisk
- It can be considered True or False – whichever is more *convenient* for the circuit

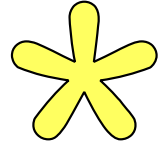

Spring 2020


Sacramento State - Cook - CSc 28

62

62

Karnaugh Maps and Don't Care

- We can construct a Karnaugh Map like before
- Except the squares corresponding to don't care outputs are marked (with an asterisk)

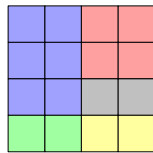

Spring 2020

Sacramento State - Cook - CSc 28

63

63

Karnaugh Maps and Don't Care

- Then, when outlining blocks, we can (at our convenience) consider the "don't care" squares as either 0 or 1
- Since we want to make the largest outlines possible, we will sometimes consider a don't care to be true, and sometimes false

Spring 2020

Sacramento State - Cook - CSc 28

64

64

Example

- We want to guarantee that the output of a circuit is 1 if both inputs are 1
- And 0 when both inputs are 0
- But otherwise we do not care

Spring 2020

Sacramento State - Cook - CSc 28

65

65

Example

a	b	out
0	0	0
0	1	*
1	0	*
1	1	1


Spring 2020

Sacramento State - Cook - CSc 28

66

66


K-Map For The Example

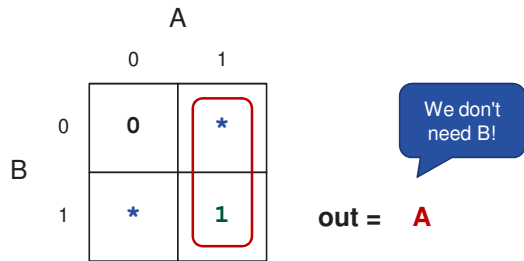

Spring 2020 Sacramento State - Cook - CSc 28 67

67


... or we can do this

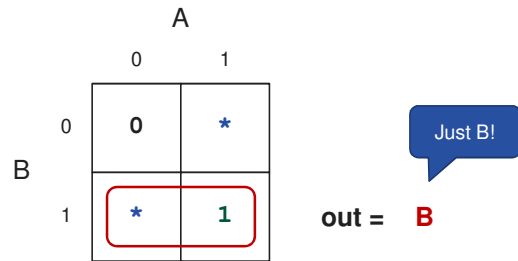

Spring 2020 Sacramento State - Cook - CSc 28 68

68

Four-Variable (with Don't Care)

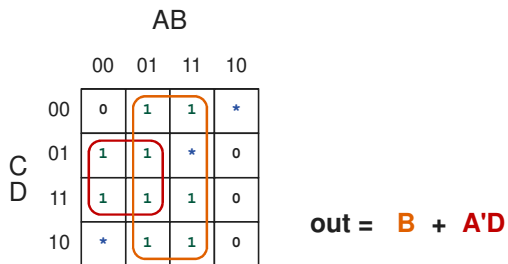

Spring 2020 Sacramento State - Cook - CSc 28 69

69



Functional Completeness

Just How Much Do We Need?

70

Functional Completeness

- We can construct a circuit for any Boolean expression using **and** / **or** / **not**
- This means the set of gates {and, or, not} is *functionally complete*



Spring 2020 Sacramento State - Cook - CSc 28 71

71

Function Completeness

- However, we don't need all three gates
- DeMorgan's laws shows us that we can construct:
 - an OR using an AND
 - and AND using an OR



Spring 2020 Sacramento State - Cook - CSc 28 72

72

We Don't Need Or!

- So {and, not} are also complete because by DeMorgan's Law:
 $x + y = (x'y)'$
- So, any expression that can be written using {and, or, not} can be written using just {and, not}



Spring 2020

Sacramento State - Cook - CSc 28

73

73

or... We Don't Need And!

- Also {or, not} is functionally complete since $xy = (x'+y)'$
- So, any expression that can be written using {and, or, not} can be written using just {or, not}



Spring 2020

Sacramento State - Cook - CSc 28

74

74

Functional Completeness

- So, are any of the singular sets {and}, {or}, {not} functionally complete?
- In other words, can and/or/not all be converted into a single type of gate?
- No.** Neither {and} or {or} can be converted to a {not}

Spring 2020

Sacramento State - Cook - CSc 28

75

75

NAND

- So, is there a gate that can, alone, be functional complete?
- What about NAND (negated And)?
 - $x \text{ nand } y = (xy)'$
 - Note: the NAND gate is not implemented with an AND gate and a NOT gate. It just has the same truth table as $(xy)'$

Spring 2020

Sacramento State - Cook - CSc 28

76

76

NAND

- To show that {nand} is functionally complete, we need to show that we can implement {and, or, not} using it
- The result would be greatly beneficial!
 - we would have to just construct 1 gate to create any circuit
 - this would greatly aid construction

Spring 2020

Sacramento State - Cook - CSc 28

77

77

Not → Nand

Converting not to nand:

$$\begin{aligned}
 x' &= x' \\
 &= (xx)' && \text{Idempotent} \\
 &= x \text{ nand } x && \text{nand format}
 \end{aligned}$$

We can implement NOT by using a NAND.
Both input will be x


Spring 2020

Sacramento State - Cook - CSc 28

78

78

Not → Nand

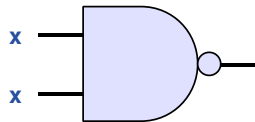

5/7/2020 Sacramento State - Cook - CSc 28 - Spring 2018 79

79

Or → Nand

Note: $x' = x \text{ nand } x$


$$\begin{aligned} x + y &= x + y \\ &= (x'y')' && \text{DeMorgan} \\ &= x' \text{ nand } y' && \text{nand format} \\ &= (x \text{ nand } x) \text{ nand } (y \text{ nand } y) \end{aligned}$$

Last proof let us convert NOT into NAND

Spring 2020 Sacramento State - Cook - CSc 28 80

80

Or → Nand

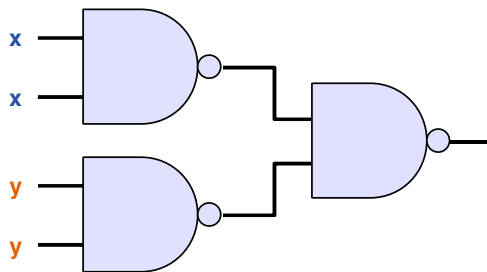

5/7/2020 Sacramento State - Cook - CSc 28 - Spring 2018 81

81

And → Nand

Note: $x' = x \text{ nand } x$


$$\begin{aligned} xy &= xy \\ &= ((xy)')' && \text{Involution} \\ &= (x \text{ nand } y)' && \text{Negate nand} \\ &= (x \text{ nand } y) \text{ nand } (x \text{ nand } y) \end{aligned}$$

Last proof let us convert NOT into NAND

Spring 2020 Sacramento State - Cook - CSc 28 82

82

And → Nand

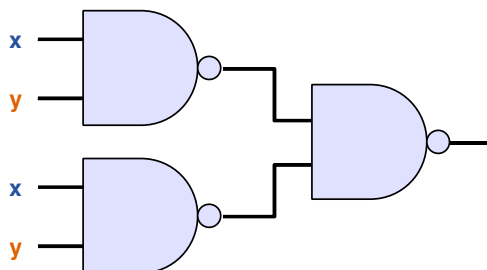

5/7/2020 Sacramento State - Cook - CSc 28 - Spring 2018 83

83

Summary

- The expressions below show that nand can be used to implement NOT, OR, AND
- So, we can just use NAND since it is *functionally complete*


$$\begin{aligned} x' &= x \text{ nand } x \\ xy &= (x \text{ nand } y) \text{ nand } (x \text{ nand } y) \\ x + y &= (x \text{ nand } x) \text{ nand } (y \text{ nand } y) \end{aligned}$$

Spring 2020 Sacramento State - Cook - CSc 28 84

84

How Hardware Works

- Also NOR is functionally complete
- $P \text{ NOR } Q = (P + Q)'$
- Hardware can alternatively use this gate rather than NAND

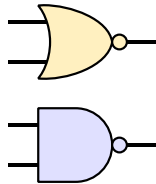

Spring 2020


Sacramento State - Cook - CSc 28

85

85

How Hardware Works

- If our hardware can just implement NAND or NOR, then we can create a circuit with just one gate
- In fact, many fabrication processes use only NAND or NOR gates

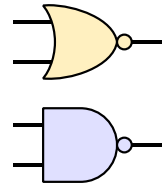

Spring 2020

Sacramento State - Cook - CSc 28

86

86