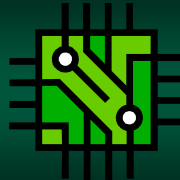


Circuits

Part 11

1




Circuits

Boolean Hardware

2

Circuits

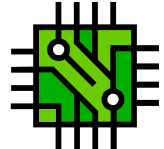
- Boolean algebra gives designers tools to design & analyze complex solutions
- Can we create hardware that performs solutions?
- Can electronic circuits allow Boolean logic to exist in the physical world?



Spring 2020 Sacramento State - Cook - CSc 28 3

3

Two Bit Multiplier? Can we make it?

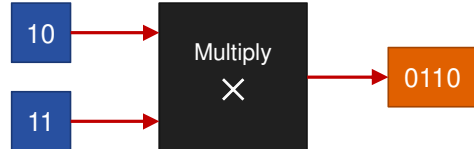

Spring 2020 Sacramento State - Cook - CSc 28 4

4

Designing It

- To design a circuit that multiplies two 2-bit numbers, we can use Boolean algebra
- We need to figure the logic – given that bits of 1 and 0 will map directly to truth values
- The result of the algebra will be the desired output

Spring 2020 Sacramento State - Cook - CSc 28 5


5

It Takes the Following Skills

1. Design a truth-table to represent the different inputs and the desired output
2. Convert the truth-table into a Boolean function
3. Simplify the Boolean function
4. Finally, convert it into a circuit

Spring 2020 Sacramento State - Cook - CSc 28 6

6

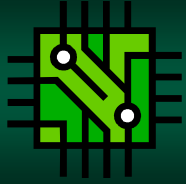


Gates

Boolean Hardware

7

Gates

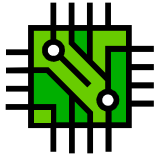- Electronic devices are made up of *gates*
- Gates take in two inputs and produce a single output
- This is how hardware is used to implement Boolean logic (or any logic)




Spring 2020 Sacramento State - Cook - CSc 28 8

8

Gates

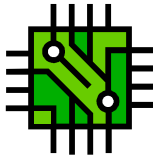- Gates can be combined into circuits with *any number of input wires* and a single output wire
- We will chain these together much like subexpressions can be combined into larger expressions



Spring 2020 Sacramento State - Cook - CSc 28 9

9


Graphical Representation

- Gates are typically represented using graphical shapes – much like flowcharts
- There are two different competing symbol standards
- We will use the standard, distinct, symbols rather than the IEC (European) ones

Spring 2020 Sacramento State - Cook - CSc 28 10

10


Or Gate

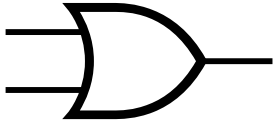

Spring 2020 Sacramento State - Cook - CSc 28 11

11


And Gate

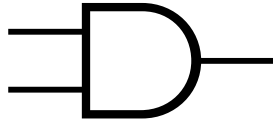

Spring 2020 Sacramento State - Cook - CSc 28 12

12

Not Gate

 


Spring 2020

Sacramento State - Cook - CSc 28

13

13

Exclusive Or Gate (aka XOR)

 

Spring 2020

Sacramento State - Cook - CSc 28

14

14

Some Other Gate Symbols

- There are also gate symbols for negated operators
- I won't use these much in class, but it's good to be aware of them (since they are quite common in computer engineering)
- For each, note the circle on the output line – it means "not"


Spring 2020

Sacramento State - Cook - CSc 28

15

15

Not Or Gate (aka NOR)

 

Spring 2020

Sacramento State - Cook - CSc 28

16

16

Not And Gate (aka NAND)




Spring 2020

Sacramento State - Cook - CSc 28

17

17

Not Exclusive Or Gate (aka XNOR)

 


Spring 2020

Sacramento State - Cook - CSc 28

18

18




Computer Engineering Notation

Same thing, different paint job

19

Computer Engineering Notation


- Gates, used to computer engineering, form a Boolean Algebra
- i.e. they can define the three operations (and, or, not) and share the same axioms



20

Computer Engineering Notation


- The notation used in computer engineering is a *tad different* that what we have covered
- ... and certainly different than any programming language you have used



21

Computer Engineering Notation

- But is serves the same purpose
- And, not surprisingly, it works better for writing expressions in this discipline




22

Computer Engineering Notation

1	≡	T
0	≡	F
*	≡	∧
+	≡	∨
!	≡	¬

23

Commutative Law

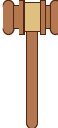


$$x + y \equiv y + x$$

$$x * y \equiv y * x$$

24

Identity Law

 

$$x * 1 \equiv x$$

$$x + 0 \equiv x$$


Spring 2020

Sacramento State - Cook - CSc 28

25

25

Complement Law

 

$$x * x' \equiv 0$$

$$x + x' \equiv 1$$


Spring 2020

Sacramento State - Cook - CSc 28

26

26

Distributive Law

 

$$x * (y + z) \equiv (x * y) + (x * z)$$

$$x + (y * z) \equiv (x + y) * (x + z)$$


Spring 2020

Sacramento State - Cook - CSc 28

27

27

Associative Law

 

$$(x + y) + z \equiv x + (y + z)$$

$$(x * y) * z \equiv x * (y * z)$$


Spring 2020

Sacramento State - Cook - CSc 28

28

28

Absorption Law

 

$$x * (x + y) \equiv x$$

$$x + (x * y) \equiv x$$


5/5/2020

Sacramento State - Cook - CSc 28 - Spring 2018

29

29

Idempotent Law

 

$$x * x \equiv x$$

$$x + x \equiv x$$


Spring 2020

Sacramento State - Cook - CSc 28

30

30

Involution Law

 

$$x'' \equiv x$$


Spring 2020

Sacramento State - Cook - CSc 28

31

31

Domination Law

 

$$x + 1 \equiv 1$$

$$x * 0 \equiv 0$$


Spring 2020

Sacramento State - Cook - CSc 28

32

32

DeMorgan's Law

 

$$(x * y)' \equiv x' + y'$$


$$(x + y)' \equiv x' * y'$$

Spring 2020

Sacramento State - Cook - CSc 28

33

33

 


Converting Boolean to Circuits

From Logic to Wires

34

Converting Boolean to Circuits

- Converting from Boolean to circuits maintains a *one-to-one* correspondence between gates and operators in the equation
- But, given an *arbitrary* Boolean expression, how do we realize a circuit for it?

 

Spring 2020


Sacramento State - Cook - CSc 28

35

35

Steps

- Choose the last operation evaluated
- Draw a gate and hook up its output
- Goto 1 until all operations have associated gates
- Attach the expression inputs

 


Spring 2020

Sacramento State - Cook - CSc 28

36

36

$$((a + b) * c)'$$

 


Spring 2020

Sacramento State - Cook - CSc 28

37

37

 


Converting Circuits to Boolean

From Logic to Wires

38

Converting Circuits to Boolean

- The other direction is easy too
- Any circuit can be realized as a Boolean expression using the same basic algorithm

 

Spring 2020

Sacramento State - Cook - CSc 28

39

39

Converting Circuits to Boolean

1. Pick a wire that has known Boolean values
2. Write on the wire a Boolean expression for its value
3. Goto 1 until all wires are complete
4. Circuit's expression written on the circuit's output wire


Spring 2020

Sacramento State - Cook - CSc 28

40

40

Example Circuit

 

Spring 2020

Sacramento State - Cook - CSc 28

41

41